

## Practical 5

### Logic Gates

NOTE: Use of internet is permitted **only** to access software website, calculators are permitted and your answers must include worked solutions. If you require extra sheet(s) please write your name and student number at the top of each additional sheet.

<https://logic.ly/>

### Part A

#### Objective

Understand various logic gates


1. Draw a labelled Gate Symbol, Functional Notation and truth table for the gates listed in the table below:

Inputs		Output(s) Truth Table				
A	B	AND	OR	XOR	NAND	NOR
0	0	0	0	0	1	1
0	1	0	1	1	1	0
1	0	0	1	1	1	0
1	1	1	1	1	0	0
Gate Symbol						
Functional Notation		$A \wedge B$	$A \vee B$	$\neg(A \equiv B)$	$\neg(A \& B)$	$\neg(A \parallel B)$

## Practical 5

### Logic Gates

2. Construct the logic circuit below using Lab Logic and detail the functional notation and truth table for a two input **AND** gate.

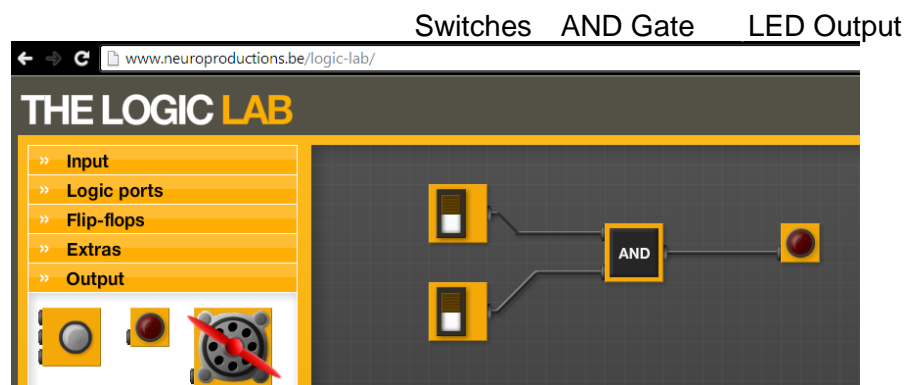

**Practical 5**  
**Logic Gates**

**Part B**

**Objective**

Understand the construction of Logic Gates from various combinations of logic gates

1. Using Lab Software prove that combining an **AND** and a **NOT** constructs a **NAND** Gate


**NOTE:** solution must be demonstrated to Lecturer prior to leaving laboratory

Demonstrated to lecturer	Yes	No
--------------------------	-----	----

## Practical 5

### Logic Gates

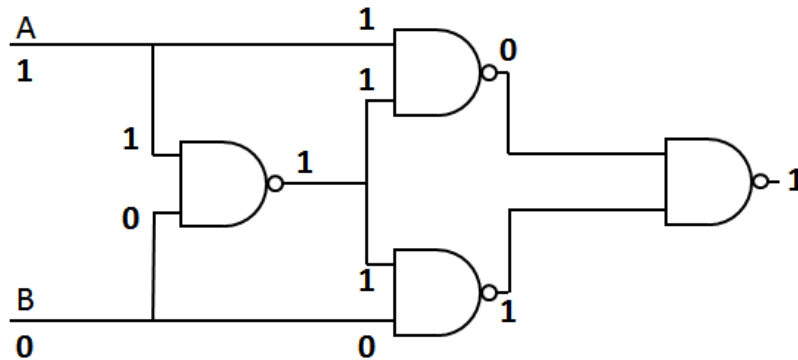2. Prove using Lab Software and a truth table that the circuit below is a XOR Gate. Place an LED on the output of the constructed circuit.



**NOTE:** solution must be demonstrated to Lecturer prior to leaving laboratory

Inputs		
A	B	XOR
0	0	
0	1	
1	0	
1	1	

Demonstrated to lecturer	Yes	No
--------------------------	-----	----

3. Prove DeMorgan's Law  $\neg(A \wedge B) = \neg A \vee \neg B$  using Lab Software

Demonstrated to lecturer	Yes	No
--------------------------	-----	----


**Practical 5**  
**Logic Gates**

**Part C**


**Objective**

- a. Understand the construction of Logic Circuits from various combinations of Logic Gates.
- b. Record the truth tables for the circuits below
- c. Suggest what these circuits could be used for

1

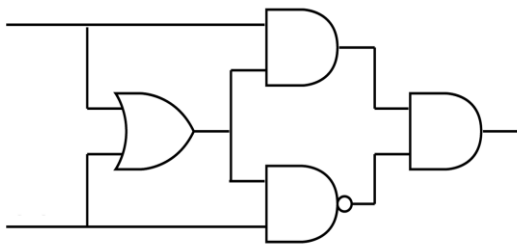


2

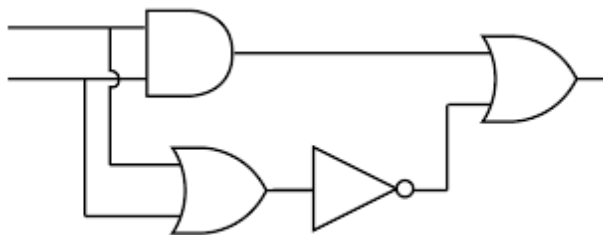

Practical 5

Logic Gates

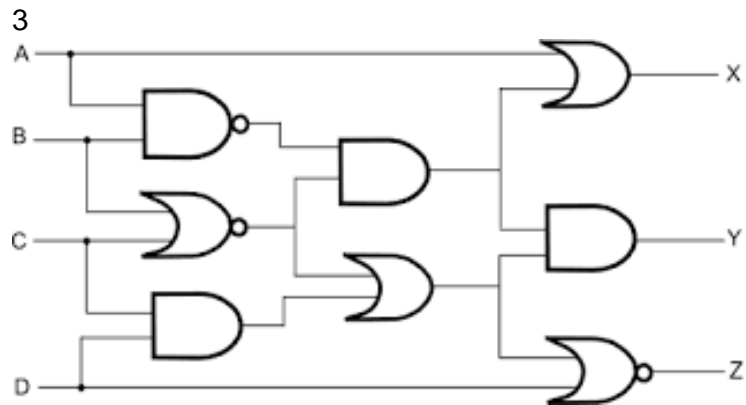

Hand up this practical report at the end of session and ensure it has been checked

Student Name		Student Number	
Date		Checked	
Group	A / B		